

Comprehensive Project Report: Magnetic Polarity Detector Using Hall-Effect Sensors

Supervised By: Dr. Nour Eldin Eng. Ehab Ahmed

Team Members: Mostafa Hatem, Yousef Abdallah, Mriam Mansour, Menna Alrahman Mohamed

1. Project Summary and Objectives

The Magnetic Polarity Detector is a functional electronic system designed to accurately identify the North and South poles of permanent magnets and indicate the relative strength of the magnetic field.

This project leverages the fundamental principles of the Hall Effect. By utilizing Hall-effect sensors (like the digital A3144 or analog SS49E), the circuit translates unseen magnetic forces into clear, visual signals using Light Emitting Diodes (LEDs).

1.1 Project Objectives

- **Primary Objective:** To design and build a reliable circuit capable of distinguishing between magnetic North and South poles using visual indicators.
- **Secondary Objective:** To demonstrate the physical principle of the Hall Effect through practical electronic application.
- **Tertiary Objective:** To analyze the mathematical relationship between magnetic field strength, current, and output voltage, and explore analog field strength detection via LED brightness variation.

2. Deep Scientific Background: The Hall Effect

2.1 Theoretical Concept and Lorentz Force

The foundation of this project rests on the Hall Effect phenomenon, discovered by Edwin Hall in 1879. The principle states that when an electrical current flows through a conductor or semiconductor material, and that material is simultaneously exposed to a magnetic field perpendicular to the current flow, a measurable voltage difference emerges across the transverse sides of the material.

When charge carriers (electrons or holes) move through the conductor at a drift velocity (v_d), the applied magnetic field exerts a force on them, known as the **Lorentz force**. The equation for this force is:

$$\vec{F} = q(\vec{v}_d \times \vec{B})$$

Where:

- $\vec{F}$ is the Lorentz force vector

- q is the charge of the particle (e.g., -1.602×10^{-19} C for an electron)
- $\vec{v}_d$ is the drift velocity vector of the particle
- $\vec{B}$ is the magnetic field vector

This force pushes the charge carriers to one side of the material, creating a localized accumulation of charge. This charge imbalance establishes an electric field ($\vec{E}_H$) that opposes further charge migration. Equilibrium is reached when the electric force equals the magnetic force:

$$q\vec{E}_H = q(\vec{v}_d \times \vec{B})$$

The resulting potential difference across the transverse axis is the **Hall Voltage**.

2.2 Hall Voltage and Hall Coefficient

The magnitude of the generated Hall Voltage (V_H) can be calculated using the following formula:

$$V_H = \frac{IB}{nqt}$$

Where:

- I is the current flowing through the material
- B is the magnetic field strength (magnetic flux density)
- n is the charge carrier density
- q is the elementary charge
- t is the thickness of the material

This relationship is often simplified using the **Hall Coefficient** (R_H), defined as $R_H = \frac{1}{nq}$. Therefore, the voltage can also be expressed as:

$$V_H = R_H \frac{IB}{t}$$

Semiconductors are typically used for Hall sensors instead of standard metals because they possess a much smaller charge carrier density (n), which results in a significantly larger, more easily measurable Hall Voltage (V_H).

3. Hardware and Detailed Components Analysis

Below is the comprehensive bill of materials and functional breakdown required for assembly:

Component	Quantity	Function in Circuit
-----------	----------	---------------------

Hall Effect Sensor (A3144)	2	Digital switch. Detects specific magnetic pole and sinks current.
Hall Effect Sensor (SS49E)	1 (Alternative)	Analog linear sensor. Outputs varying voltage based on field strength.
9V Battery & Clip	1	Main power supply.
Voltage Regulator (LM7805)	1	Drops 9V input to a stable 5V (V_{cc}) to protect sensitive ICs.
Resistor (10kΩ)	2	Pull-up resistors to keep the open-collector output HIGH when inactive.
Resistor (220Ω)	2	Current-limiting resistors to prevent LED thermal runaway.
LED (1 Red, 1 Green)	2	Visual indicators. Red = South/North (depending on configuration).
Transistor (BC547 NPN)	1 (Optional)	Amplifies the analog signal from the SS49E to drive the LEDs directly.
Breadboard & Jumper Wires	1 set	Solderless prototyping platform.

3.1 Sensor Internal Architecture

- **A3144 (Digital):** Inside this IC, there is a Hall voltage generator, a small-signal amplifier, a Schmitt trigger (to provide a clean, jitter-free ON/OFF switching threshold), and an open-collector NPN transistor output.
 - *Activation:* 30 to 80 Gauss.
 - *Deactivation:* 10 to 60 Gauss (includes hysteresis to prevent flickering).
- **SS49E (Analog):** Lacks the Schmitt trigger. Instead, the small-signal amplifier is routed directly to the output pin. The output voltage rests at $\approx 2.5V$ (half of V_{cc}) when no magnetic field is present. A South pole increases the voltage towards $5V$, while a North pole decreases it towards $0V$.

4. Polarity Detection Architectures

4.1 Architecture A: Dual Digital Sensors (A3144)

Because the A3144 is unipolar, it only responds to the South pole of a magnet facing its branded side. To detect both poles, the circuit requires two A3144 sensors placed **back-to-back**:

- **Sensor A (Front-facing):** Triggers when the South pole approaches.
- **Sensor B (Rear-facing):** Triggers when the North pole approaches.

4.2 Architecture B: Single Analog Sensor (SS49E) + Transistor

Using an SS49E allows for field strength indication (LED brightness). The sensor output is fed to the base of a BC547 NPN transistor.

- When V_{out} increases (South pole), the base current (I_B) increases, causing the collector current (I_C) to increase proportionally ($I_C = \beta \cdot I_B$), brightening the LED.
- When V_{out} decreases (North pole), the transistor cuts off, turning the LED off. (A more complex dual-transistor push-pull circuit is required to light a separate LED for the North pole using this single sensor).

5. Circuit Design and Mathematical Modeling

5.1 Thermal Dissipation in Voltage Regulation

The LM7805 linear regulator drops the 9V battery voltage to 5V. The excess voltage is converted into heat. If both LEDs are active simultaneously (worst-case scenario), drawing approximately $20mA$ each, plus the quiescent current of the sensors ($\approx 10mA$), the total load is $I_{load} = 50mA = 0.05A$.

$$P_{dissipated} = (V_{in} - V_{out}) \times I_{load}$$

$$P_{dissipated} = (9V - 5V) \times 0.05A = 0.20W$$

Since $0.20W$ is well below the 7805's $1W$ un-heatsinked limit, thermal failure is not a risk.

5.2 LED Current Limiting Calculation

The A3144 has an open-collector output, meaning it connects the output pin to Ground when activated. To light an LED, it is connected between the 5V rail and the output pin.

Using a standard red LED with a forward voltage drop (V_f) of $2.0V$, we calculate the required limiting resistor (R) to achieve a safe $15mA$ ($0.015A$) current:

$$R = \frac{V_{cc} - V_f}{I_{desired}}$$

$$R = \frac{5V - 2.0V}{0.015A} = \frac{3.0V}{0.015A} = 200\Omega$$

A standard 220Ω resistor is chosen as the closest safe value, yielding an actual current of:

$$I_{actual} = \frac{3.0V}{220\Omega} \approx 13.6mA$$

6. Implementation Steps and Troubleshooting

6.1 Assembly Procedure

1. **Power Delivery:** Connect the 9V battery to the LM7805 regulator input. Route the 5V output to the breadboard power rail. Connect grounds commonly.
2. **Sensor Placement:** Insert two A3144 sensors into the breadboard, orienting them physically opposite to each other.
3. **Sensor Wiring:**
 - Pin 1 (V_{cc}): Connect to +5V.
 - Pin 2 (GND): Connect to Ground.
 - Pin 3 (OUT): Connect to a $10k\Omega$ pull-up resistor (to +5V).
4. **Indicator Wiring:** Connect the Anode of the Red LED to +5V through a 220Ω resistor. Connect its Cathode to Pin 3 of Sensor A. Repeat for the Green LED on Sensor B.

6.2 Troubleshooting Guide

- **Issue: LEDs are always ON.**
 - *Cause:* The open-collector output requires the LED to be placed between V_{cc} and the output pin. If placed between the output pin and Ground, it will remain off or behave erratically. Ensure correct wiring polarity.
- **Issue: LEDs never turn ON.**
 - *Cause:* The magnetic field may be too weak (below the 80 Gauss threshold). Test with a stronger neodymium magnet rather than a weak fridge magnet. Alternatively, the LED polarity is reversed.
- **Issue: Voltage regulator becomes too hot to touch.**
 - *Cause:* A short circuit exists on the 5V rail. Immediately disconnect the battery and check for bridged connections.

7. Testing and Calibration Procedure

1. **Quiescent State Verification:** Apply 9V power. Both LEDs must remain completely OFF in the absence of external magnetic fields. Measure the output pins with a multimeter; they should read approximately $5V$ due to the pull-up resistors.
2. **South Pole Activation:** Bring the known South pole of a permanent magnet close to Sensor A. The Red LED must illuminate sharply. The multimeter on Pin 3 should drop to $< 0.4V$.
3. **North Pole Activation:** Flip the magnet. Present the North pole to Sensor B. The Green LED must illuminate sharply, and the Red LED must turn OFF.
4. **Hysteresis Observation:** Slowly move the magnet away from the sensor. Note the exact distance where the LED turns OFF. Move it closer again and note where it turns ON. The "ON" distance will be slightly closer than the "OFF" distance—this is the physical manifestation of the Schmitt trigger's hysteresis.

8. Real-World and Industrial Applications

The principles demonstrated in this project are ubiquitous in modern technology:

- **Brushless DC (BLDC) Motor Commutation:** The most common application. Three Hall sensors are spaced 120° apart inside the motor to detect the position of the magnetic rotor, allowing the controller to fire the correct electromagnet coils in sequence.
- **Automotive Anti-Lock Braking Systems (ABS):** A magnetic reluctor wheel rotates with the car axle. A Hall sensor detects the passing magnetic teeth to calculate exact wheel speed.
- **Non-Destructive Material Testing:** Detecting invisible micro-fractures in metal pipes by inducing a magnetic field and using Hall sensors to map field leakages caused by the cracks.
- **Current Sensing:** Devices like the ACS712 pass a high current near a Hall sensor. Because electrical current generates a magnetic field proportional to the amperage (Ampere's Law), the sensor measures the current without physically touching the high-voltage wire (galvanic isolation).

9. Future Extensions and Advanced Configurations

This foundational circuit serves as a stepping stone for highly advanced instrumentation:

- **Microcontroller Integration (Arduino/Raspberry Pi):** By reading the analog output of an SS49E sensor using an ADC (Analog-to-Digital Converter) pin on a microcontroller, one can calculate the exact Gauss value using software math and display it on an LCD screen.
- **3D Spatial Tracking:** By arranging three linear Hall sensors orthogonally (X, Y, and Z axes), the system can determine the exact 3-dimensional coordinate position and orientation of a moving magnet in real-time.
- **Digital Tachometer:** Attaching a small magnet to a rotating shaft (like a fan or motor) and using a single A3144 sensor. By counting the number of LOW pulses per second (Hz) via a